

## Questions with Answer Keys

MathonGo

## Q1 - 2024 (01 Feb Shift 1)

Two identical capacitors have same capacitance  $C$ . One of them is charged to the potential  $V$  and other to the potential  $2V$ . The negative ends of both are connected together. When the positive ends are also joined together, the decrease in energy of the combined system is :

(1)  $\frac{1}{4}CV^2$


(2)  $2CV^2$

(3)  $\frac{1}{2}CV^2$

(4)  $\frac{3}{4}CV^2$
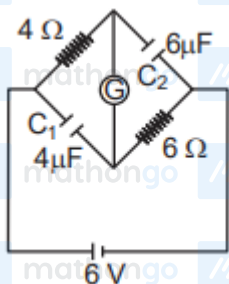
## Q2 - 2024 (01 Feb Shift 2)

A galvanometer ( $G$ ) of  $2\Omega$  resistance is connected in the given circuit. The ratio of charge stored in  $C_1$  and  $C_2$  is :



(1)  $\frac{2}{3}$


(2)  $\frac{3}{2}$

(3) 1

(4)  $\frac{1}{2}$
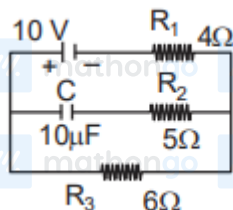
## Q3 - 2024 (01 Feb Shift 2)

In an electrical circuit drawn below the amount of charge stored in the capacitor is           $\mu C$ .



Do you want to practice these PYQs along with PYQs of JEE Main from 2002 till 2024?


[Click here to download MARKS App](#)

## Questions with Answer Keys

MathonGo

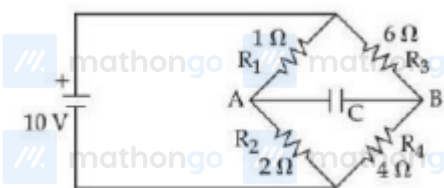Q4 - 2024 (27 Jan Shift 1)

The charge accumulated on the capacitor connected in the following circuit is \_\_\_\_\_  $\mu\text{C}$  ( Given  $C = 150\mu\text{F}$  )



Q5 - 2024 (29 Jan Shift 1)

A capacitor of capacitance  $100\mu\text{F}$  is charged to a potential of 12 V and connected to a  $6.4\text{mH}$  inductor to produce oscillations. The maximum current in the circuit would be :

- (1) 3.2 A
- (2) 1.5 A
- (3) 2.0 A
- (4) 1.2 A

Q6 - 2024 (29 Jan Shift 1)

A  $16\Omega$  wire is bent to form a square loop. A 9 V battery with internal resistance  $1\Omega$  is connected across one of its sides. If a  $4\mu\text{F}$  capacitor is connected across one of its diagonals, the energy stored by the capacitor will be  $\frac{x}{2}\mu\text{J}$ . where  $x =$  \_\_\_\_\_

Q7 - 2024 (30 Jan Shift 1)

A capacitor of capacitance  $C$  and potential  $V$  has energy  $E$ . It is connected to another capacitor of capacitance  $2C$  and potential  $2V$ . Then the loss of energy is  $\frac{x}{3}E$ , where  $x$  is \_\_\_\_\_

Q8 - 2024 (31 Jan Shift 1)

A parallel plate capacitor with plate separation 5 mm is charged up by a battery. It is found that on introducing a dielectric sheet of thickness 2 mm, while keeping the battery connections intact, the capacitor draws 25%

Do you want to practice these PYQs along with PYQs of JEE Main from 2002 till 2024?

[Click here to download MARKS App](#)

## Questions with Answer Keys

MathonGo

more charge from the battery than before. The dielectric constant of the sheet is \_\_\_\_\_

Do you want to practice these PYQs along with PYQs of JEE Main from 2002 till 2024?

[Click here to download MARKS App](#)

## MathonGo

**Answer Key**

Do you want to practice these PYQs along with PYQs of JEE Main from 2002 till 2024?

**Click here to download MARKS App**

## Solutions

MathonGo

Q1

$$V_C = \frac{q_{\text{net}}}{C_{\text{net}}} = \frac{CV + 2CV}{2C}$$


$$V_C = \frac{3V}{2}$$

Loss of energy

$$= \frac{1}{2} CV^2 + \frac{1}{2} C(2V)^2 - \frac{1}{2} 2C \left( \frac{3V}{2} \right)^2$$

$$= \left( \frac{CV^2}{4} \right)$$

Q2

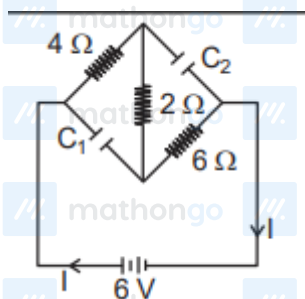

In steady state

$$R_{\text{eq}} = 12\Omega$$

$$I = \frac{6}{12} = 0.5 \text{ A}$$

$$\text{P.D across } C_1 = 3 \text{ V}$$


$$\text{P.D across } C_2 = 4 \text{ V}$$

$$q_1 = C_1 V_1 = 12\mu\text{C}$$

$$q_2 = C_2 V_2 = 24\mu\text{C}$$

$$\frac{q_1}{q_2} = \frac{1}{2}$$

Q3

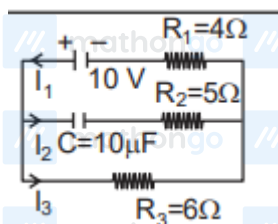

Do you want to practice these PYQs along with PYQs of JEE Main from 2002 till 2024?

[Click here to download MARKS App](#)

## Solutions

MathonGo

In steady state there will be no current in branch of capacitor, so no voltage drop across  $R_2 = 5\Omega$

$$I_2 = 0$$

$$I_1 = I_3 = \frac{10}{4+6} = 1 \text{ A}$$


$$V_{R_3} = V_c + V_{R_2} \quad V_{R_2} = 0$$

$$I_3 R_3 = V_c$$

$$V_c = 1 \times 6 = 6 \text{ volt}$$

$$q_c = CV_c = 10 \times 6 = 60\mu\text{C}$$

Q4

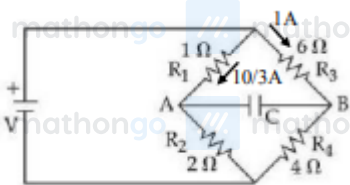

$$V_A + \frac{10}{3}(1) - 6(1) = V_B$$

$$V_A - V_B = 6 - \frac{10}{3} = \frac{8}{3} \text{ volt}$$

$$Q = C(V_A - V_B)$$

$$= 150 \times \frac{8}{3} = 400\mu\text{C}$$

Q5

By energy conservation

$$\frac{1}{2}CV^2 = \frac{1}{2}LI_{\max}^2$$

$$I_{\max} = \sqrt{\frac{C}{L}}V$$

$$= \sqrt{\frac{100 \times 10^{-6}}{6.4 \times 10^{-3}}} \times 12$$

$$= \frac{12}{8} = \frac{3}{2} = 1.5 \text{ A}$$


Q6

Do you want to practice these PYQs along with PYQs of JEE Main from 2002 till 2024?

[Click here to download MARKS App](#)

## Solutions

MathonGo

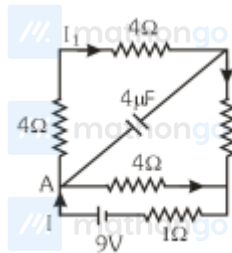

$$I = \frac{V}{R_{eq}} \quad I = \frac{V}{R_{eq}} = \frac{9}{1 + \frac{12 \times 4}{12 + 4}} = \frac{9}{4}$$

$$I_1 = \frac{9}{4} \times \frac{4}{16} = \frac{9}{16}$$

$$V_A - V_B = I_1 \times 8 = \frac{9}{16} \times 8 = \frac{9}{2} V$$

$$\therefore U = \frac{1}{2} \times 4 \times \frac{81}{4} \mu J$$

$$\therefore U = \frac{81}{2} \mu J$$

$$\therefore x = 81$$

Q7

$$\begin{aligned} \text{Energy loss} &= \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2 \\ &= \frac{2}{3} \cdot E \end{aligned}$$

$$\therefore x = 2$$

Q8

Without dielectric

$$Q = \frac{A\epsilon_0}{d} V$$

with dielectric

$$Q = \frac{A\epsilon_0 V}{d - t + \frac{t}{K}}$$

given

$$\frac{A\epsilon_0 V}{d - t + \frac{t}{K}} = (1.25) \frac{A\epsilon_0 V}{d}$$

$$\Rightarrow 1.25 \left( 3 + \frac{2}{K} \right) = 5$$

$$\Rightarrow K = 2$$

Do you want to practice these PYQs along with PYQs of JEE Main from 2002 till 2024?

[Click here to download MARKS App](#)